LED Foldies



Origami LED Lampions

Electric circuits don't necessarily need to be soldered – they can also be folded!

The small lanterns mix electrical engineering with the ancient art of paper folding.

Want to invent a circuit yourself?

Would you like to try alternative origami forms? Or do you have other ideas how the origami foldings could work with LEDs?

Just try it out:

- fold your origami shape
- mark on the folded shape with a pencil where the LED legs and the battery are going
- open the shape
- on the open sheet, draw the connections from battery trough the LED back to the other side of the battery.

Pay attention to how many creases you cross - the less the better.

Prevent short circuits: the connections should not touch each other and themselves when folded again!

Paper-Circuitry

You can find many projects with electric circuits on paper under the term "paper circuitry" online. It's also interesting to experiment with other materials, i.e. copper bands or even conductive ink, which allows to draw circuits directly on paper.

What you need

- square folding paper, 60-70g/m² (i.e. origami paper, but gift wrap paper does work as well)
 - Size: 20 x 20 cm
- Printout of the circuit (p. 7/8)
- 1LED
- 1 cell battery (CR2032)
- strong tinfoil
- scissors, glue

to attach in trees

- thin wire
- pliers

► https://learn.sparkfun.com/ tutorials/the-great-big-guideto-paper-circuits

Step by step



Fold the paper like indicated and open it again.



Transfer the shape of the circuit on tinfoil and cut it out.



Glue the tinfoil circuit on the paper.

Ironing the circuit!

If you have access to a laser printer, you can use it to print the circuit shape directly on your origami paper.

You can then iron the cut tinfoil directly onto the paper. No gluing necessary.



Fold the paper again, insert the LED*.




Fix the legs of the LED with adhesive tape for stability.



Finish the folding.



Inflate the balloon.

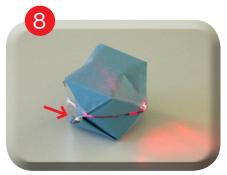

Insert the battery. Maybe flip the battery to match the polarity of the LED.



Try other shapes: Pikachu, bird, rabbit - or invent another shape?

* the LED can be turned inwards (like shown), but can point outwards as well (works fine with the rabbit).





HeK (House of electronic Arts Basel), 2018





This work is available under Creative Commons
Attribution-NonCommercial-ShareAlike 4.0
International (CC BY-NC-SA 4.0)

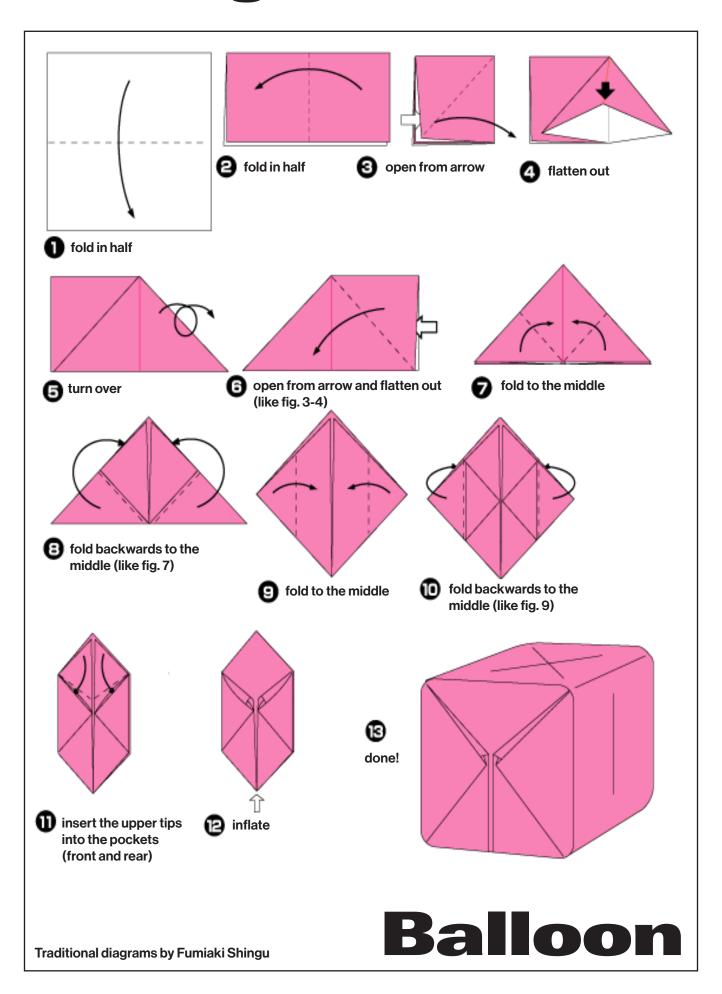This worksheet is based on a blogpost by Leonore Edmann, Evil Mad Scientist Laboratories, USA www.evilmadscientist.com



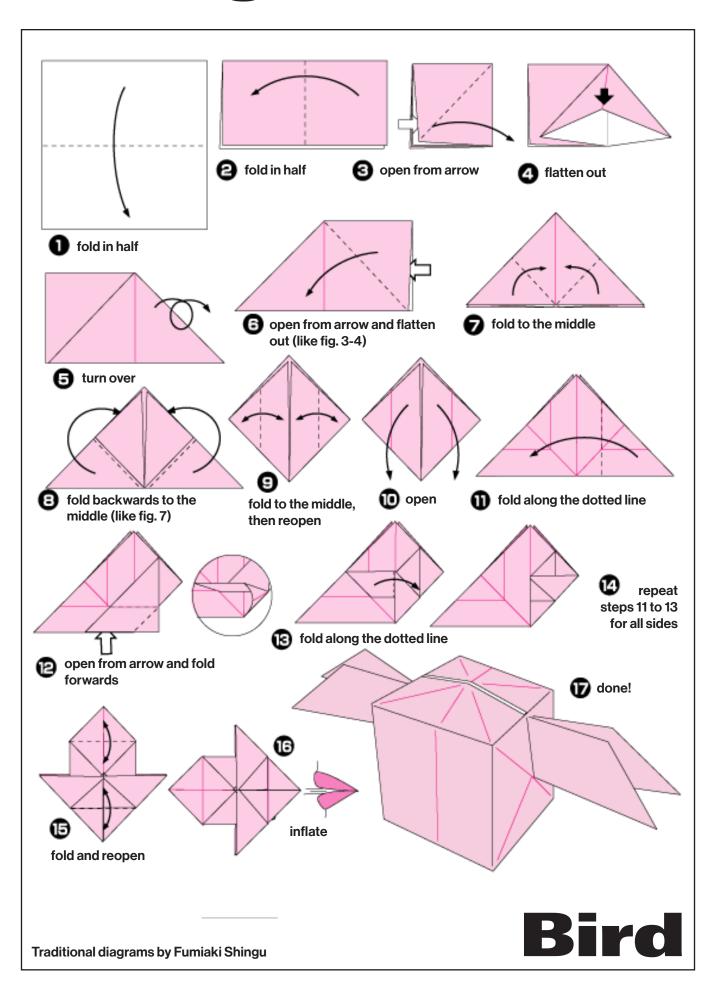

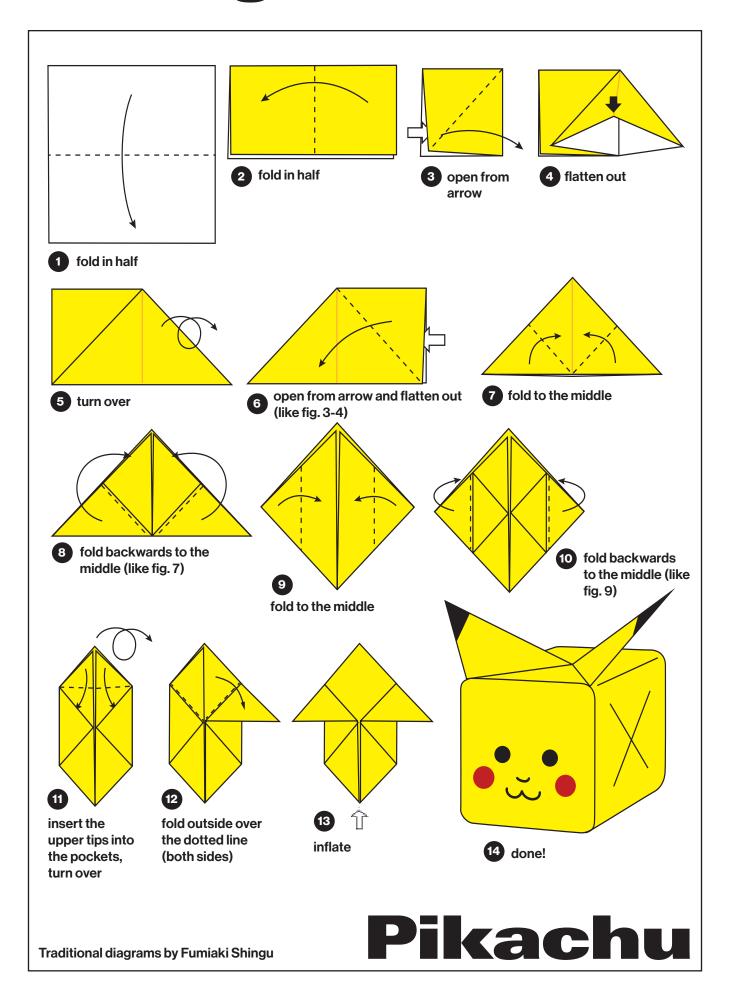


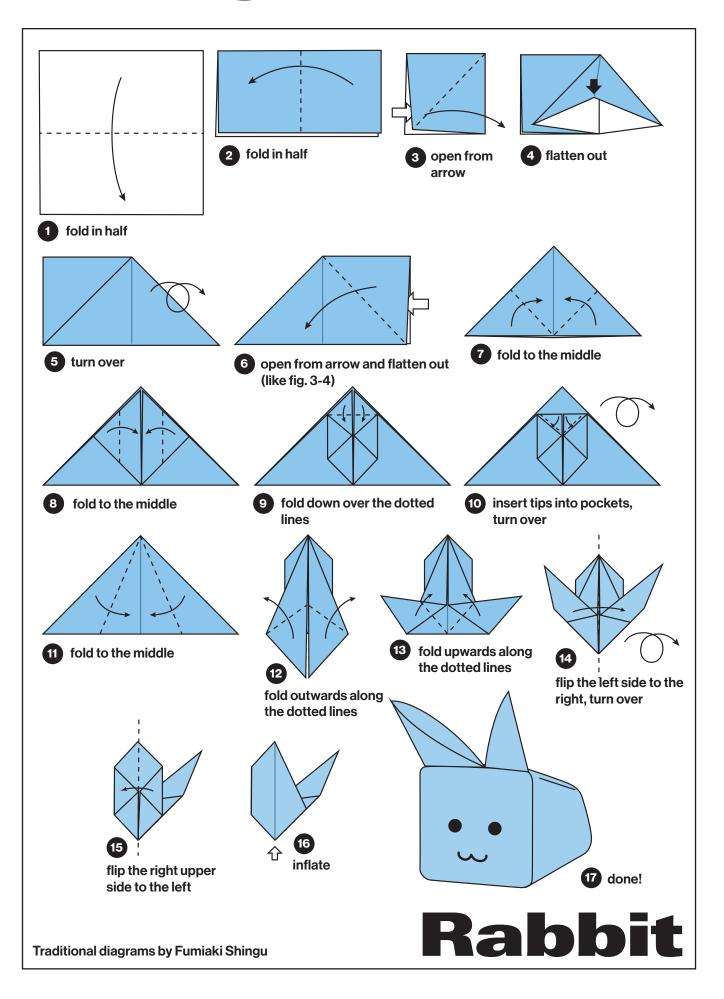

LED-foldie circuit

Template for transfer Size 20 x 20 cm


For balloon, Pikachu and rabbit

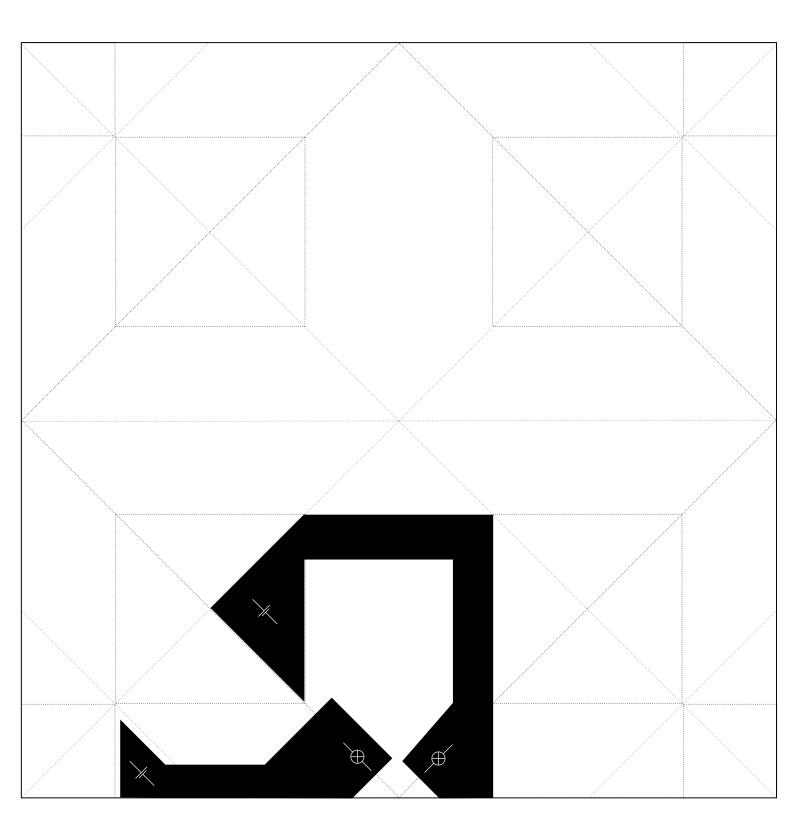

LED-foldie circuit

Template for transfer Size 20 x 20 cm


For bird

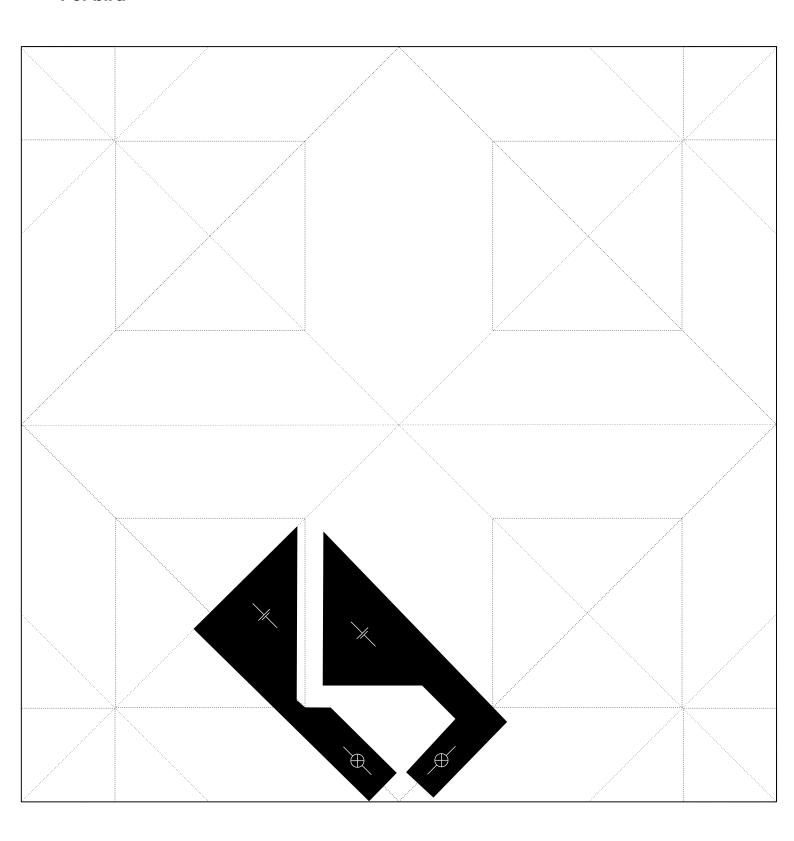

LED-foldie circuit

For printing on folding paper (and ironing tinfoil on it) Size 20 x 20 cm

For balloon, Pikachu and bird

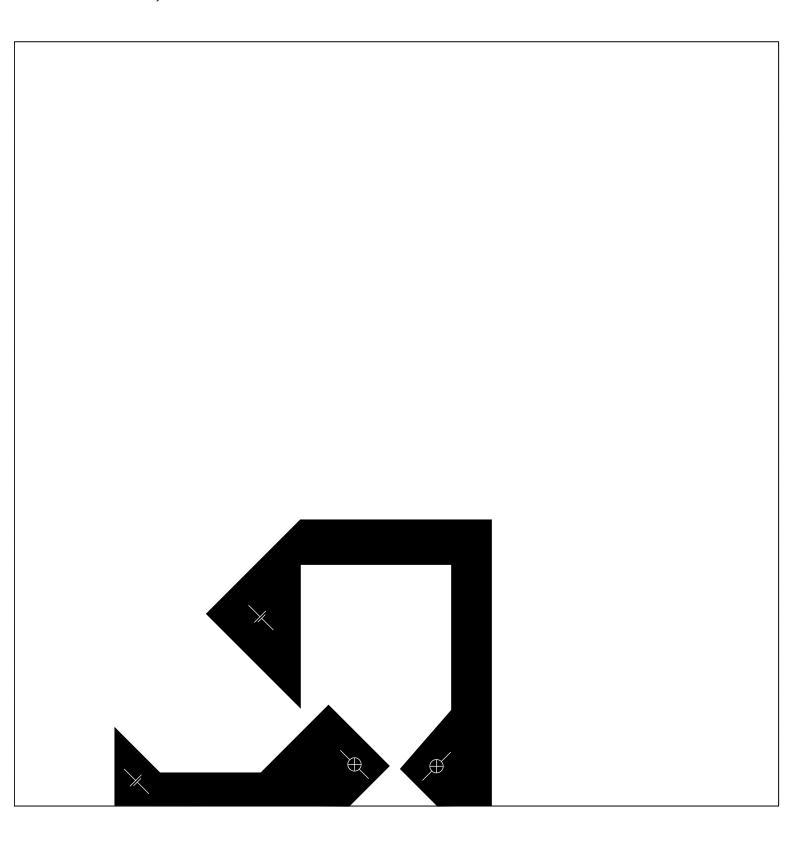

For laserprinter only, does not work with inkjet printer!